

Power in a Balanced Three-Phase System

- ❑ To find total power in a balanced system
 - Determine power in one phase
 - Multiply by three

- You can also use single-phase equivalent in power calculations
 - Power will be power for just one phase



Three-Phase Active (**Average**) Power

□ Active power per phase = $V_{\phi} I_{\phi}$ x power factor

□ Total active power = $3 V_{\phi} I_{\phi}$ x power factor

$$P = 3V_{\phi} I_{\phi} \cos \theta$$

➤ If I_L and V_L are rms values for line current and line voltage respectively. Then for delta (Δ) connection: V_{ϕ}

= V_L and $I_{\phi} = I_L / \sqrt{3}$. therefore: $P = \sqrt{3} V_L I_L \cos \theta$

➤ For star connection (Y) : $V_{\phi} = V_L / \sqrt{3}$ and $I_{\phi} = I_L$. therefore:

$$P = \sqrt{3} V_L I_L \cos \theta$$



Three-Phase Instantaneous Power

Instantaneous Phase Voltages

$$v_{an}(t) = V_m \sin(\omega t)$$

$$v_{bn}(t) = V_m \sin(\omega t - 120^\circ)$$

$$v_{cn}(t) = V_m \sin(\omega t - 240^\circ)$$

$$v_{an}(t) = \sqrt{2}V \sin \omega t$$

$$v_{bn}(t) = \sqrt{2}V \sin(\omega t - 120^\circ)$$

$$v_{cn}(t) = \sqrt{2}V \sin(\omega t - 240^\circ)$$

Instantaneous Phase Currents

$$i_a(t) = I_m \sin(\omega t - \theta)$$

$$i_b(t) = I_m \sin(\omega t - \theta - 120^\circ)$$

$$i_c(t) = I_m \sin(\omega t - \theta - 240^\circ)$$

$$i_a(t) = \sqrt{2}I \sin(\omega t - \theta)$$

$$i_b(t) = \sqrt{2}I \sin(\omega t - 120^\circ - \theta)$$

$$i_c(t) = \sqrt{2}I \sin(\omega t - 240^\circ - \theta)$$



Three-Phase Instantaneous Power

✓ Instantaneous Power

$$p(t) = v(t)i(t)$$

➤ Therefore, the instantaneous power supplied to each phase is:

$$p_a(t) = v_{an}(t)i_a(t) = 2VI \sin(\omega t) \sin(\omega t - \theta)$$

$$p_b(t) = v_{bn}(t)i_b(t) = 2VI \sin(\omega t - 120^\circ) \sin(\omega t - 120^\circ - \theta)$$

$$p_c(t) = v_{cn}(t)i_c(t) = 2VI \sin(\omega t - 240^\circ) \sin(\omega t - 240^\circ - \theta)$$

■ Since

$$\sin \alpha \sin \beta = \frac{1}{2} [\cos(\alpha - \beta) - \cos(\alpha + \beta)]$$



Three-Phase Instantaneous Power

▪ Therefore

$$p_a(t) = VI [\cos \theta - \cos(2\omega t - \theta)]$$

$$p_b(t) = VI [\cos \theta - \cos(2\omega t - 240^\circ - \theta)]$$

$$p_c(t) = VI [\cos \theta - \cos(2\omega t - 480^\circ - \theta)]$$

➤ The total instantaneous power


$$p_{tot}(t) = p_a(t) + p_b(t) + p_c(t) = 3VI \cos \theta$$

Note that: the pulsing components cancel each other because of 120° phase shifts.

✓ For a balanced three phase circuit the instantaneous power is constant



Three-Phase Instantaneous Power

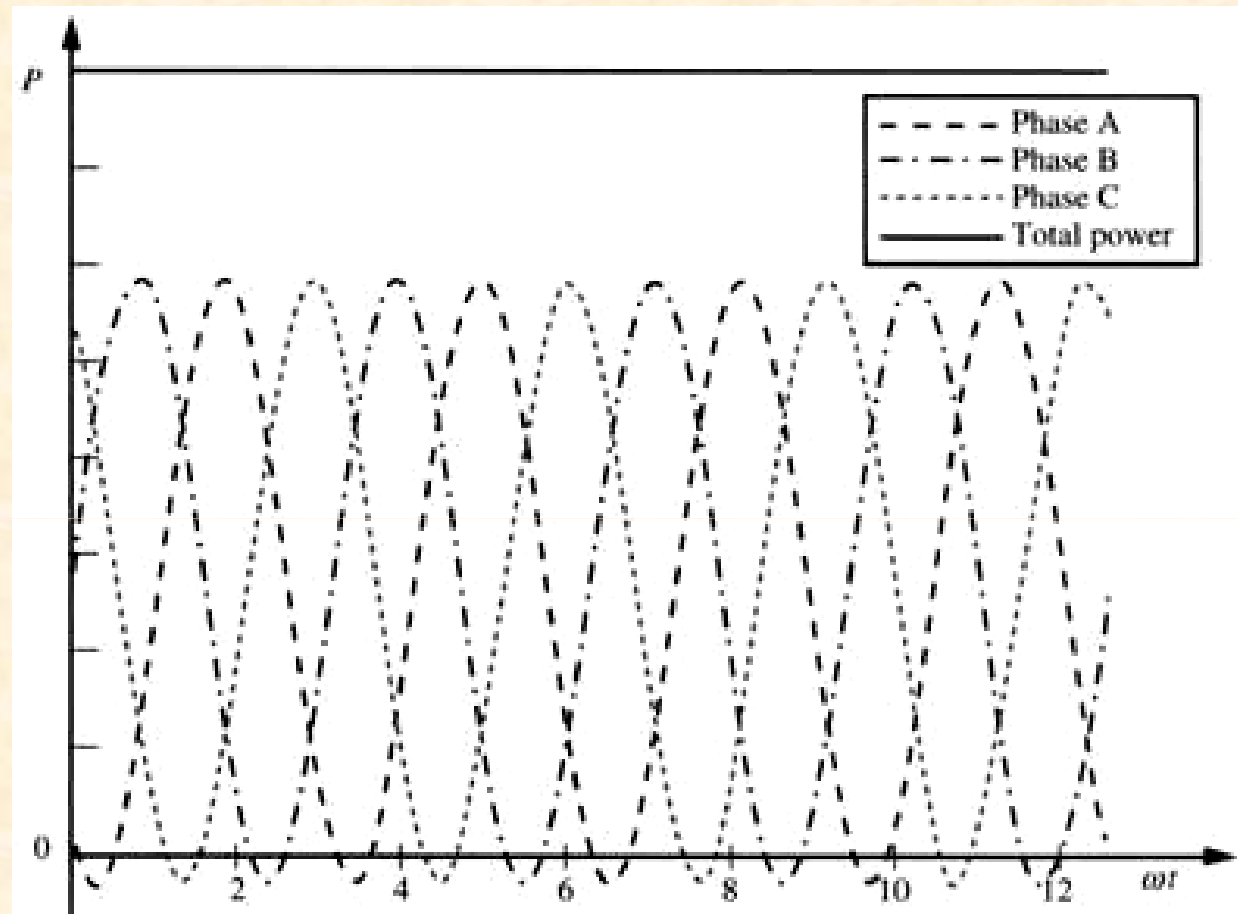


✓ power in phases
is **Time Variant**

✓ The total power supplied
to the load is **constant**



Power Relationships For a balanced Three-Phase load

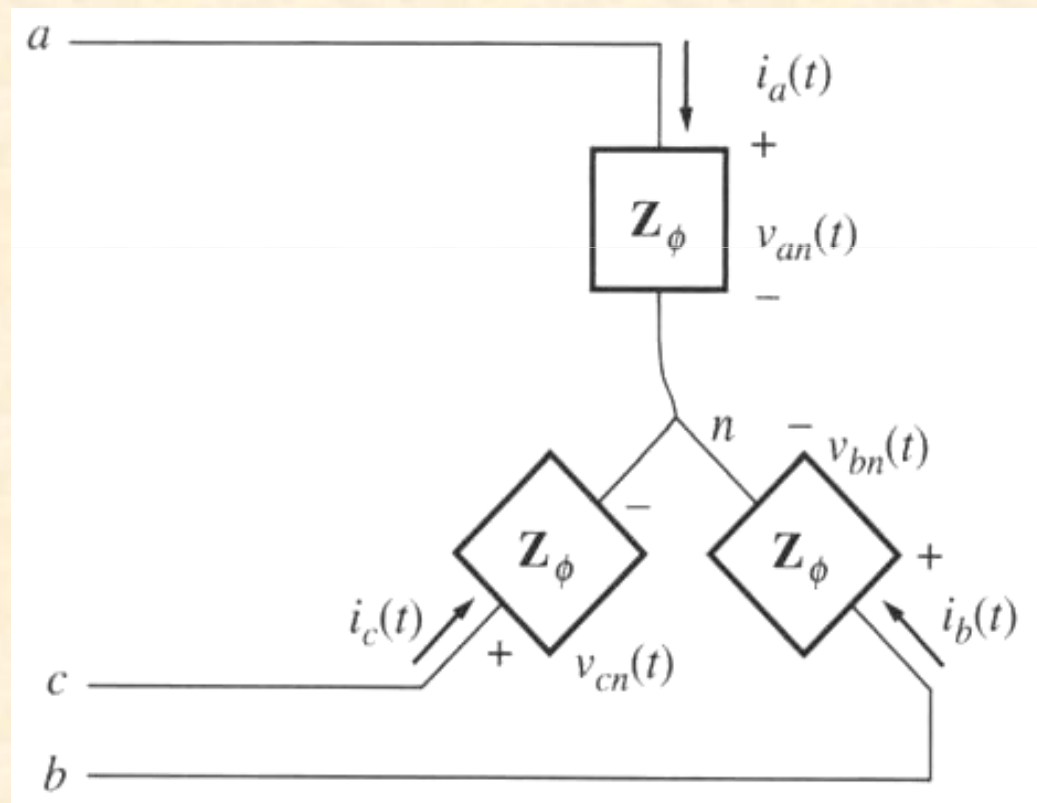- For a balanced Y-connected load with the impedance $Z_\phi = Z \angle \theta$:



Power Relationships For a balanced Three-Phase load

□ Using **Phase** quantities in each phase of a Y- or Δ -connection

✓ Real Power:

$$P = 3V_{\phi}I_{\phi} \cos \theta = 3I_{\phi}^2 Z \cos \theta \quad 3I_{\phi}^2 R$$

✓ Reactive Power:

$$Q = 3V_{\phi}I_{\phi} \sin \theta = 3I_{\phi}^2 Z \sin \theta \quad 3I_{\phi}^2 X$$

✓ Apparent Power:

$$S = 3V_{\phi}I_{\phi} = 3I_{\phi}^2 Z$$



Power Relationships For a Balanced Three-Phase load

□ Using **Line** quantities of a Y-connected Load

✓ Real Power

$$P = 3V_{\phi} I_{\phi} \cos \theta$$

➤ Since for this load $I_L = I_{\phi}$ and $V_{\phi} = V_L / \sqrt{3}$

➤ Therefore: $P = 3 \frac{V_L}{\sqrt{3}} I_L \cos \theta$

➤ Finally: $P = \sqrt{3} V_L I_L \cos \theta$



Power Relationships For a Balanced Three-Phase load

□ Using **Line** quantities of a Δ -connected Load

✓ Real Power $P = 3V_{\phi} I_{\phi} \cos \theta$

➤ Since for this load $V_L = V_{\phi}$ and $I_{\phi} = I_L / \sqrt{3}$

➤ Therefore: $P = 3 V_L \frac{I_L}{\sqrt{3}} \cos \theta$

➤ Finally: $P = \sqrt{3} V_L I_L \cos \theta$

Same as for a Y-connected load!



Power Relationships For a Balanced Three-Phase load

□ Using **Line** quantities of Y- or Δ -connection

➤ Reactive power: $Q = \sqrt{3}V_L I_L \sin \theta$

➤ Apparent power: $S = \sqrt{3}V_L I_L$

□ Note: θ is the angle between the phase voltage and the phase current – the impedance angle.

✓ Power factor is: $F_p = \cos \theta = P/S = P_\phi/S_\phi$

